



# Multiplexer and Demultiplexer

## Exercises Digital Design


### Solution vs. Hints:



While not every response provided herein constitutes a comprehensive solution, some serve as helpful hints intended to guide you toward discovering the solution independently. In certain instances, only a portion of the solution is presented.

## 1 | MUX - Multiplexer
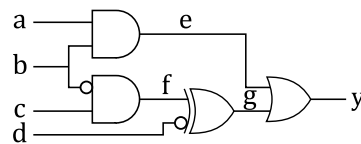
### 1.1 Creating a function with the help of Multiplexers



*mux/mux-01*



1.2 Creating a function with the help of Multiplexers

a	b	c	d	y	y'
0	0	0	0	0	$d$
0	0	0	1	1	
0	0	1	0	1	$\bar{d}$
0	0	1	1	0	
0	1	0	0	1	$\bar{d}$
0	1	0	1	0	
0	1	1	0	0	$d$
0	1	1	1	1	
1	0	0	0	1	$\bar{d}$
1	0	0	1	0	
1	0	1	0	0	$d$
1	0	1	1	1	
1	1	0	0	0	$d$
1	1	0	1	1	
1	1	1	0	1	$\bar{d}$
1	1	1	1	0	

*mux/mux-02*

1.3 Creating a function with the help of Multiplexers

1.3.1 Solution

- For  $y$  4xMux 2-1
- For  $z$  4xMux 2-1

*mux/mux-03*

1.4 Creating a function with the help of Multiplexers

- $s = \bar{c}$
  - $y = 1$
- $w = \bar{a}$
  - ...

*mux/mux-04*



## 1.5 Creating a function with the help of Multiplexers

The truthtable non simplified is:

<i>d</i>	<i>c</i>	<i>b</i>	<i>a</i>	<i>y</i>	<i>z</i>
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	1	1
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	0	1

*mux/mux-05*



## 2 | MUX - Demultiplexer

### 2.1 Demultiplexer from 1 to 8

You need 8xAND-4 + 3xNOT

*mux/demux-01*

### 2.2 Logic Circuit

You need a XNOR with 2 inputs.

*mux/demux-02*

### 2.3 Complete Operators

Multiplexer 2-1 as well as a Demultiplexer 1-2 are both complete operators.

*mux/demux-03*